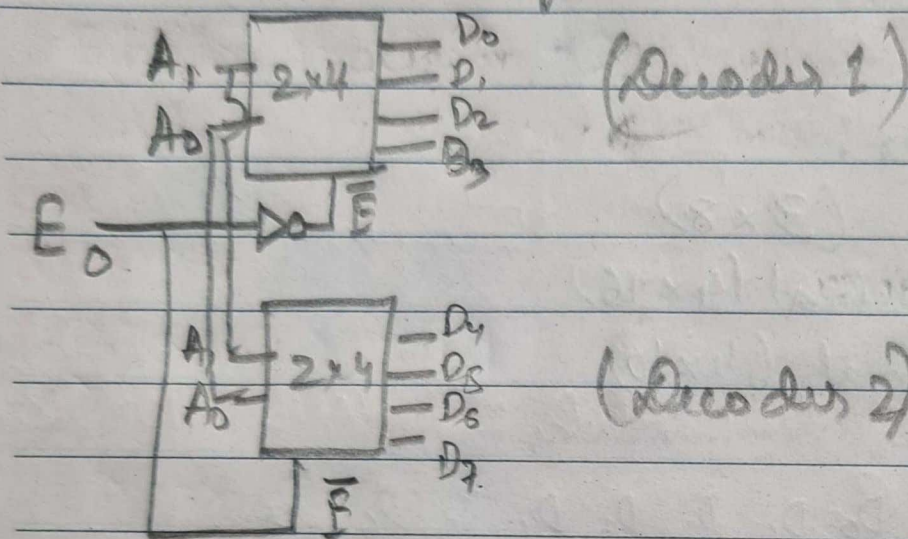


3x8 Decoder using 2x4 decoder.



	E	A_1	A_0	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
Decoder 1 is active	0	0	0	1	0	0	0	0	0	0	0
	0	0	1	0	1	0	0	0	0	0	0
	0	1	0	0	0	1	0	0	0	0	0
	0	1	1	0	0	0	1	0	0	0	0
Decoder 2 is active	1	0	0	0	0	0	0	1	0	0	0
	1	0	1	0	0	0	0	0	1	0	0
	1	1	0	0	0	0	0	0	0	1	0
	1	1	1	0	0	0	0	0	0	0	1

When enable is 0, decoder 1 is active and when enable is 1, decoder 2 is active.

Thus, we have our required 3x8 decoder using two 2x4 decoders.